

# Contents

<b>1</b>	<b>Objective</b>	<b>2</b>
<b>2</b>	<b>Specifications</b>	<b>2</b>
<b>3</b>	<b>Two stage Operational Amplifier</b>	<b>2</b>
<b>4</b>	<b>Design Specification and Calculations</b>	<b>4</b>
<b>5</b>	<b>Schematics and output</b>	<b>7</b>
5.1	Miller compensation technique . . . . .	7
5.2	Nulling resistor compensation . . . . .	9
5.3	2 stage without feedback . . . . .	11
<b>6</b>	<b>Observation</b>	<b>13</b>
<b>7</b>	<b>Results</b>	<b>14</b>
7.1	Miller compensation technique . . . . .	14
7.2	Nulling resistance technique . . . . .	14
7.3	2 stage without feedback . . . . .	14
<b>8</b>	<b>Conclusion</b>	<b>14</b>

# 1 Objective

The main objective of this experiment is design and analysis of a 2-stage opamp. The designed op-amp should have the following specifications:

- $A_v = 2000$
- $GBW = 15 \text{ Mhz}$
- $C_L = 10 \text{ pF}$
- $ICMR = 0.8V - 1.6V$
- $\text{Slew Rate} = 10V/\mu S$

# 2 Specifications

- Mosfet length of 180nm
- A bias current of 40 $\mu A$  is assumed.
- A voltage supply of 1.8V is used.

# 3 Two stage Operational Amplifier

A two-stage operational amplifier consists of a differential amplifier at the input stage, while the second stage is a high gain stage biased by the output of the differential amplifier. The first stage is a differential pair with a current mirror load. The second stage is a common source amplifier. Use a simple current source with a diode-connected PMOS load as the bias circuit. The basic circuit is shown in [Figure 1].

Gain of 1st stage:

$$A_{v1} = -g_{m1,2}(r_{o2} || r_{o4}) \quad (1)$$

Gain of 2nd stage:

$$A_{v2} = -g_{m6}(r_{o6} || r_{o7}) \quad (2)$$

Overall gain of two stage:

$$A_v = A_{v1}A_{v2} = g_{m1,2}g_{m6}(r_{o2} || r_{o4})(r_{o6} || r_{o7}) \quad (3)$$

 


Figure 1: Typical circuit for 2 stage OTA

If we look into node A, we see that:

$$r_{oA} = r_{o3} || r_{o1} || \frac{1}{g_{m3}} \approx \frac{1}{g_{m3}}$$

which is a very low value. Now we consider the nodes B and C.

$$R_1 = r_{o2} || r_{o4}$$

$$R_2 = (r_{o6} || r_{o7})$$

from the above small signal model we get

$$P_1 \approx \frac{-1}{R_1 R_2 g_{m6} C_c}$$

$$P_2 \approx \frac{-g_{m6}}{C_1 + C_2}$$

Thus as we increase  $C_c$ ,  $P_1$  moves closer to origin and thus pole splitting happens and compared to case without capacitor we will get stable value of phase margin near around 60 degree.

For stability purpose:

$$\omega_{gc} < \omega_{pc} \quad (4)$$

## 4 Design Specification and Calculations

The various steps involved in designing the circuit are listed below:

1. for a PM of 60 degree, we choose  $C_c$  such that

$$C_c > 0.22 C_L \quad (5)$$

here  $C_L$  is given as 10pF, putting this in above equation we get

$$C_c > 2.2 pF \quad (6)$$

Assume  $C_c = 2.5 pF$

2. We know slew rate is given by,

$$SR = \frac{dV_{out}}{dt} = I_5 C_c \quad (7)$$

Putting values of SR and  $C_c$  we get,

$$I_5 = 25 \mu A \quad (8)$$

3. Design for  $S_3$  from the maximum input voltage specification

$$S_3 = \frac{I_5}{K_p (V_{DD} - V_{in-max} - |V_{T3}| + V_{T1-min})^2} \quad (9)$$

where  $K_p = 70\mu A/V^2$ ,  $V_{T3} = -0.43V$

$$\frac{W_3}{L_3} = \frac{W_4}{L_4} = 4.89 \quad (10)$$

$$W_3 = W_4 = 880.2nm \quad (11)$$

4. Verify that the pole of M3 due to  $C_{gs3}$  and  $C_{gs4} = 0.67W_3L_3C_{ox}$  will not be dominant by assuming it to be greater than 10 GB

$$\frac{g_{m3}}{2g_{s3}} > 10GB \quad (12)$$

5. Design for S1(S2) to achieve the desired GB.

$$g_{m1} = GB * C_c = 235.62\mu A/V^2 \quad (13)$$

$$\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_{m1}^2}{2K_nI_1} \quad (14)$$

$$S_1 = S_2 = 8.224 \quad (15)$$

$$W_1 = W_2 = 1480.32nm \quad (16)$$

6. Using the min ICMR equation with reference to the given circuit, we get the value of  $V_{sat5}$  as :

$$V_{dsat5} = V_{in,min} - V_{gs1} - V_{ss}$$

$$V_{dsat5} = V_{in,min} - \sqrt{\frac{2I_{d1}}{\mu_n C_{ox} \frac{W_1}{L_1}}} - V_{tn1} - V_{ss}$$

Putting the necessary values we get,

$$V_{dsat5} = V_{gs5} - V_{t5} = 0.235V \quad (17)$$

Now we substituing these values in current equation for NMOS transistor M5 we get the value of W-L ratio for M5 as ,

$$\frac{W_5}{L_5} = 3.533 \quad (18)$$

$$W_5 = 603.54nm \quad (19)$$

7. Find S6 by letting the second pole (p2) be equal to 2.2 times GB and assuming that  $V_{SG4} = V_{SG6}$ .

$$\frac{W_6}{L_6} = \frac{W_4}{L_4} \frac{g_{m6}}{g_{m4}} \quad (20)$$

$$S_6 = 124.66 \quad (21)$$

$$W_6 = 31320nm \quad (22)$$

8. Calculate  $I_6$  from

$$I_6 = \frac{g_{m6}^2}{2k_6 S_6} \quad (23)$$

$$I_6 = 318.1\mu A \quad (24)$$

9. Design S7 to achieve the desired current ratios between  $I_5$  and  $I_6$

$$S_7 = (I_6/I_5)S_5 = 42.663 \quad (25)$$

$$W_7 = 7679.34nm \quad (26)$$

Putting this result in the below relation we get

$$\frac{W_8}{L_8} = \frac{W_5}{L_5} \frac{I_{d8}}{I_{d5}} \quad (27)$$

$$\frac{W_8}{L_8} = 5.36 \quad (28)$$



 


Figure 4: 3 dB frequency

 


Figure 5: phase at gain crossover frequency



## 5.2 Nulling resistor compensation

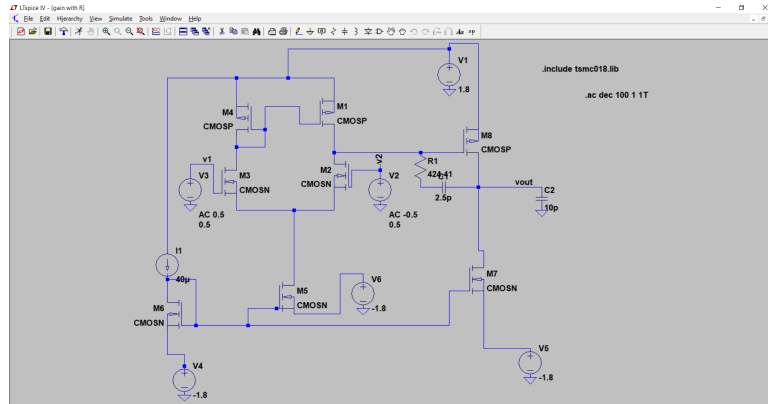


Figure 6: Schematic



Figure 7: Gain

 


Figure 8: 3 dB frequency

 


Figure 9: phase at gain crossover frequency

## 5.3 2 stage without feedback

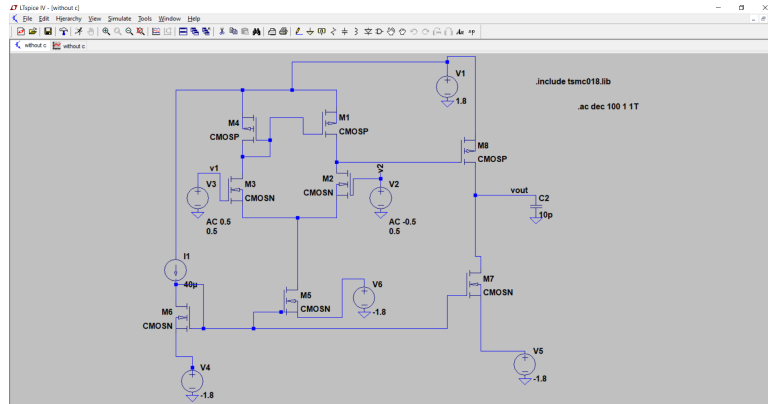


Figure 10: Schematic

 


Figure 11: Gain

 


Figure 12: 3 dB frequency

 


Figure 13: phase at gain crossover frequency

## 6 Observation

W/L ratios for all transistors							
M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	M <sub>4</sub>	M <sub>5</sub>	M <sub>6</sub>	M <sub>7</sub>	M <sub>8</sub>
8.224	8.224	4.89	124.66	3.353	124.66	42.663	5.364

Table 1:

- Value of nulling resistance

$$R_2 = \frac{1}{gm_2}$$

$$R_2 = \frac{1}{2356.2 \times 10^{-6}}$$

$$R_2 = 424.41 \Omega$$

- There is no effect on the gain of the circuit in all 3 methods  
Ideal gain =  $20 \log(2000) = 66 \text{ dB}$

Gain in dB		
Miller capacitance	Nulling resistor	2 stage without feedback
50.27 dB	50.30 dB	50.28 dB

Table 2:

BW in dB	
Miller capacitance	Nulling resistor
82.90 KHz	82.9 KHz

Table 3:

- PM with miller approximation  
PM =  $180^\circ + (-112.45^\circ) = 67.55^\circ$
- PM with nulling resistance compensation  
PM =  $180^\circ + (-105.41^\circ) = 74.59^\circ$
- Phase margin is higher in nulling resistance compensation technique ,hence stability is higher.
- PM without compensation capacitor  
 $180^\circ + (-170^\circ) = 10^\circ$  hence the stability is less.

## 7 Results

### 7.1 Miller compensation technique

- Gain =50.27dB
- Bandwidth=82.90 Khz
- Phase at Gain crossover frequency =  $-112.45^\circ$   
PM=67.55 °

### 7.2 Nulling resistance technique

- Gain=50.30dB
- Bandwidth=82.9 Khz
- Phase at Gain crossover frequency =  $-105.41^\circ$   
PM=74.59 °

### 7.3 2 stage without feedback

- Gain=50.28 dB
- Bandwidth= 4.88 Mhz
- Phase at Gain crossover frequency =  $-170^\circ$   
PM=10°

## 8 Conclusion

- The compensation capacitor helps in pole splitting.
- Pole splitting shifts the one pole (less dominant ) to the right of unity gain bandwidth frequency and dominant pole to the left.
- Because of pole splitting because of dominant pole the transfer function is like a single pole system.
- The compensation capacitor adds a right half plane zero to the system.

- The RHP zero decreases the phase margin of the system, hence decreasing the stability.
- The power consumption for miller compensation is high.
- So to improve the phase margin and hence improve stability we used a resistor in series with compensation capacitance.
- Adding series resistance reduces the need of selecting high  $g_m$ , reducing current, in turn reducing power consumption,
- The 2 stage Op-amp circuit offers high gain.
- The 2 stage Op-amp circuit has higher output voltage swing than OTA.
- The 2 stage Op-amp circuit with miller compensation technique has higher power dissipation than an OTA as  $g_m$  of mosfet where output is taken has to be approximately 10 times than the  $g_m$  on mosfet where input is given.
- The Op-amp with desired design specifications was designed.